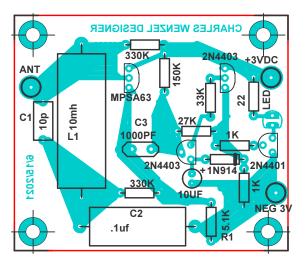
## ALVIN P. SCHMITT IMPROVED LIGHTING DETECTOR



C1 1 nf C2 33nf C3 1.5nf L1 PER NOTES ON WEB SITE R1 2.7K

The magnetic antenna version can be build on the same board with the following component changes and the coil L1 per the instructions at: techlib.com/electronics/lightingnew.HTM#magnetic